


**CSE 331**  
**COMPUTER ORGANIZATION**  
**ASSIGNMENT 3**  
**REPORT**

Name: Türker

Surname: Tercan


Student ID: 171044032

# ALU DESIGN:

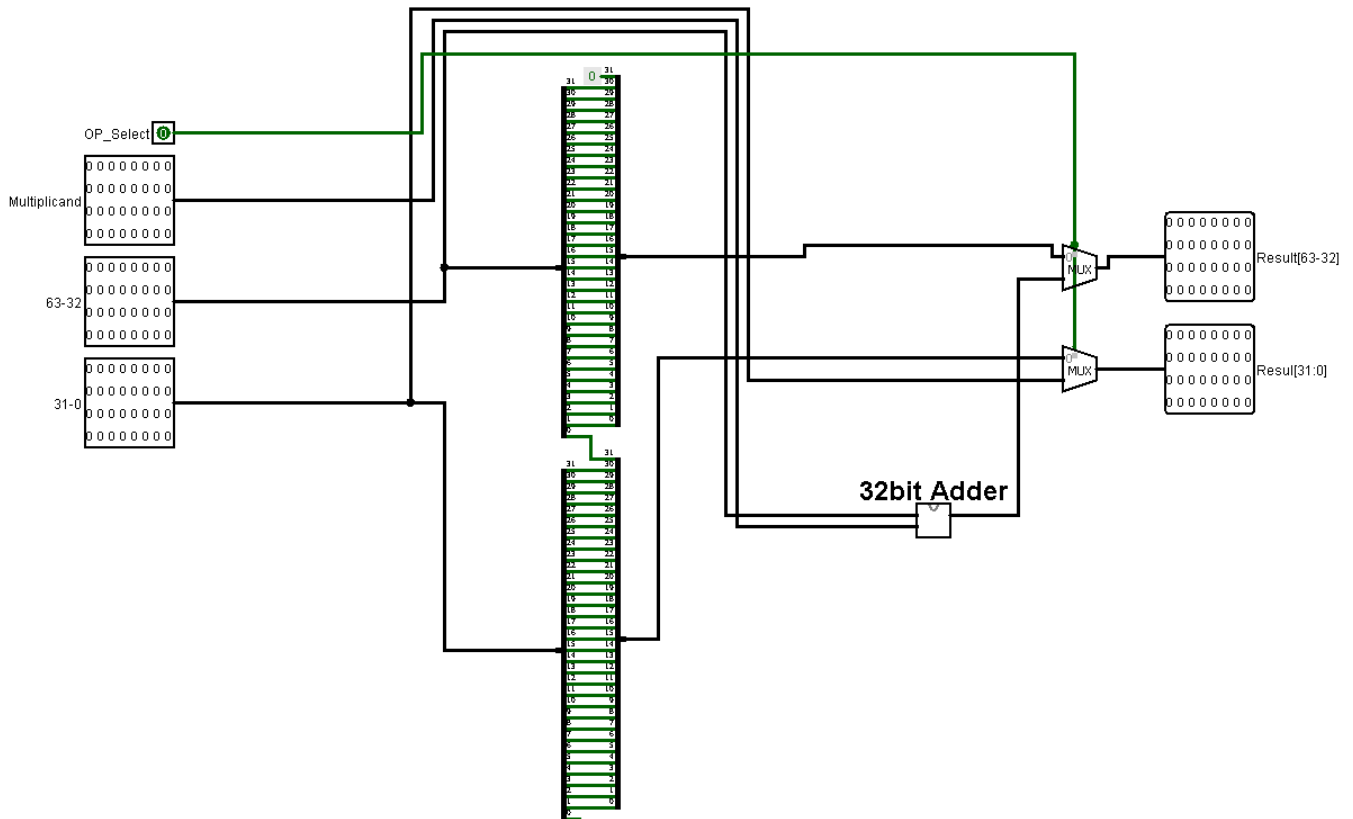


- Since we need to use this ALU just for multiplying purposes, we don't have to implement all things inside of general purpose ALUs.
- We need implement a 64-bit shifter and 32-bit adder.
- Instead of using a multiplexer to every single bit of product for shifting like you taught us during the lessons, I used two multiplexers for what operator we are doing.

## 32-bit Adder:

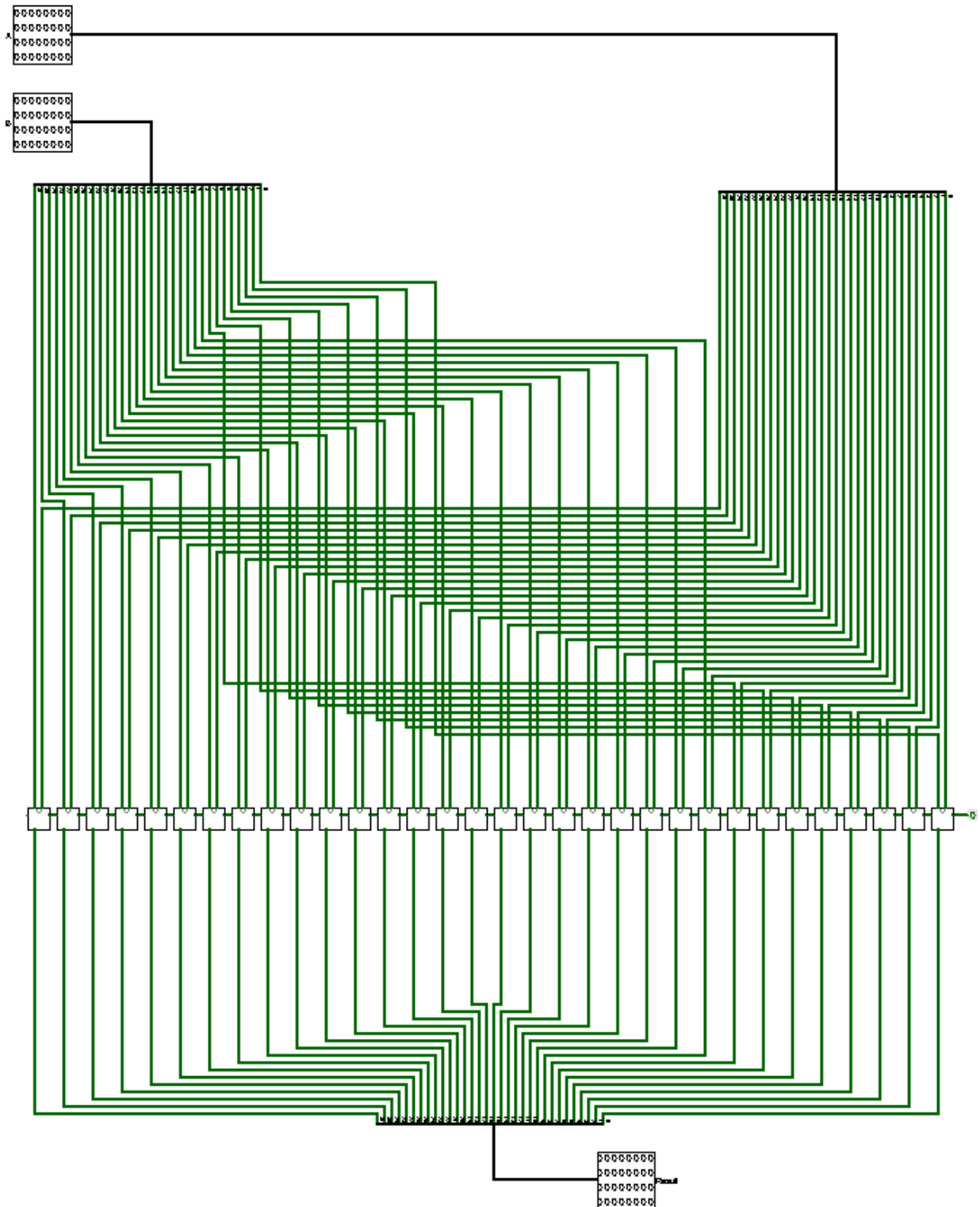




## 1-bit Adder:

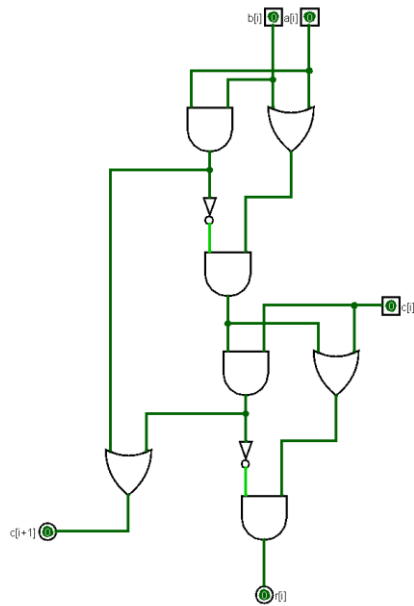

Exact copy 1-bit Adder from course slides

## Control Unit:

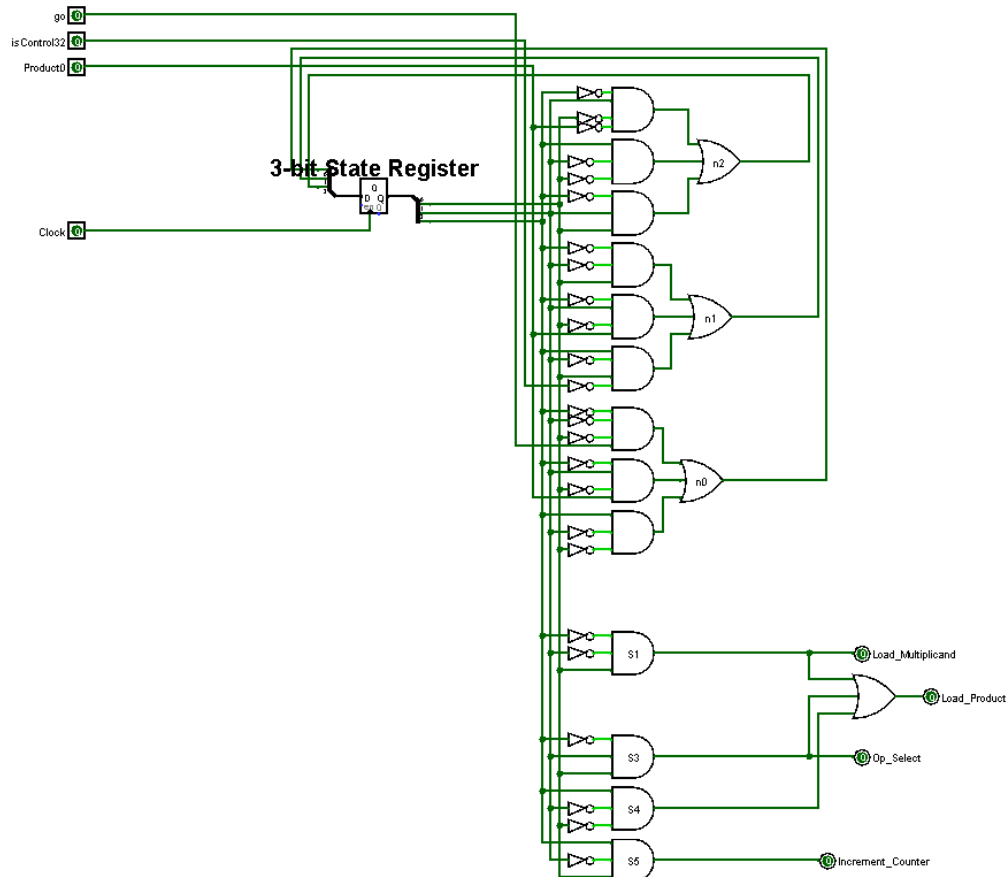

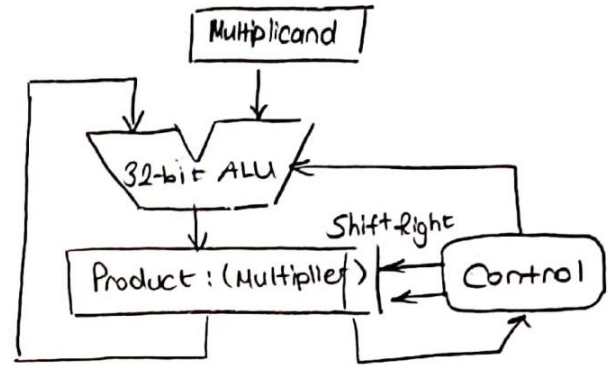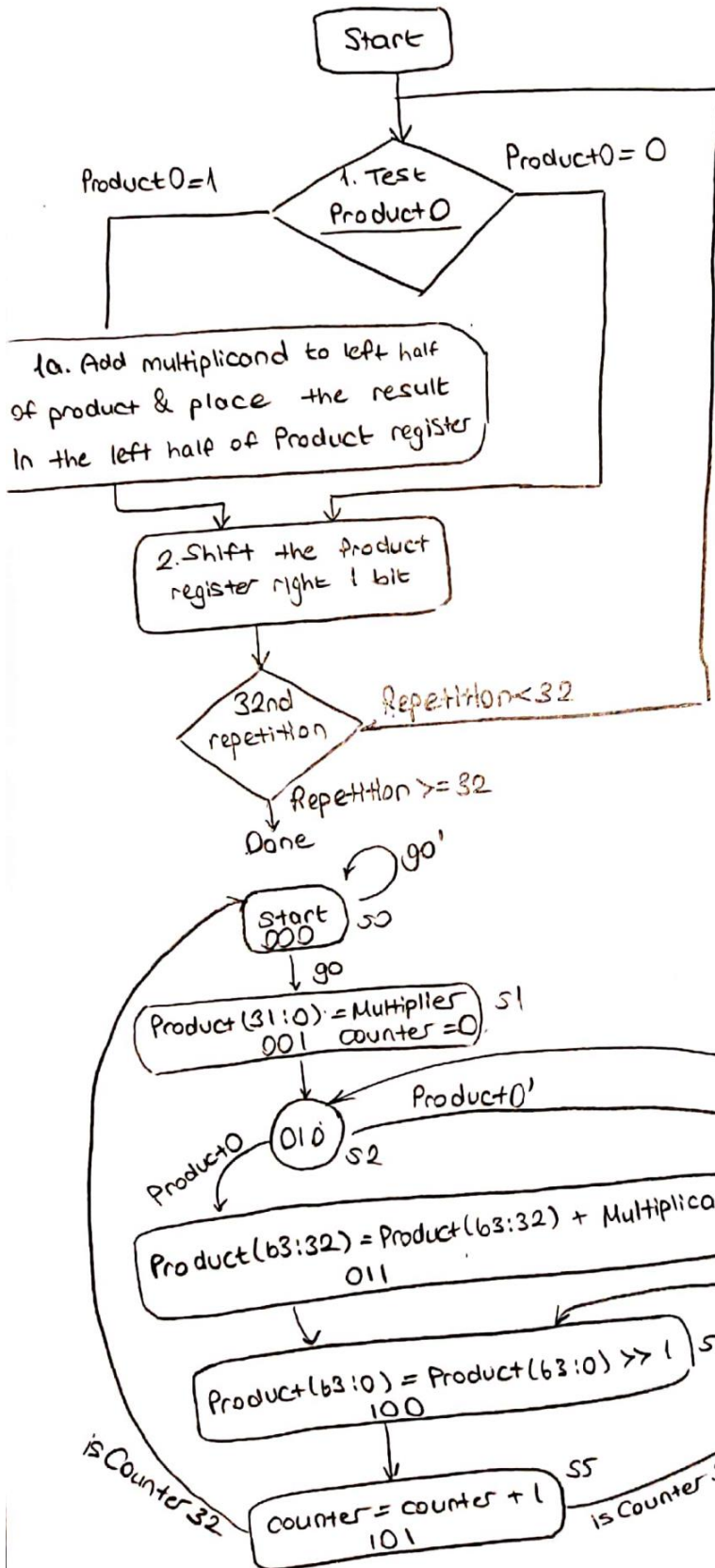

- o Multiplier must be stored at start state
- o 64-bit Product register needed
- o 5-bit counter register needed

s2	s1	s0	g0	Product0	isCounter32	n2	n1	n0
0	0	0	0	-	-	0	0	0
0	0	0	1	-	-	0	0	1
0	0	1	-	-	-	0	1	0
0	1	0	-	0	-	0	1	1
0	1	0	-	1	-	1	0	0
0	1	1	-	-	-	1	0	0
1	0	0	-	-	-	1	0	1
1	0	1	-	-	0	0	1	0
1	0	1	-	-	1	0	0	0

$$n2 = s2's1's0'Product0' + s2s1's0' + s2's1's0$$

$$s2's1's0'Product0' + s2 \text{ xor } (s1's0')$$


$$n1 = s2's1's0 + s2's1's0'Product0 - s2s1's0'isCounter32'$$

$$n0 = s2's1's0'g0 + s2's1's0'Product0' + s2s1's0'$$

s2	s1	s0	Op-select	Load-Multiplicand	Increment Counter	Reset Counter	Select Load	Load-Product
0	0	0	s0	x	0	0	0	0
0	0	1	s1	x	1	0	1	0
0	1	0	s2	x	0	0	0	1
0	1	1	s3	1	0	0	0	1
1	0	0	s4	0	0	0	0	0
1	0	1	s5	x	0	0	0	0

## Test Cases:


1-

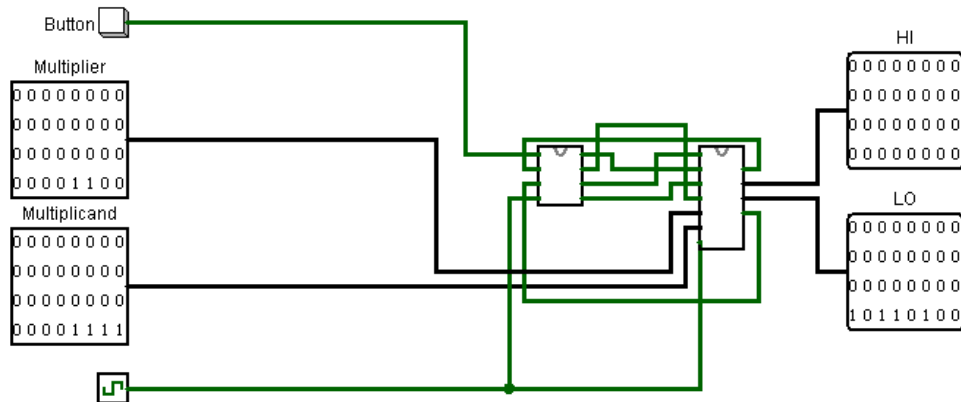

$$12 * 15 = 180$$


---

2-

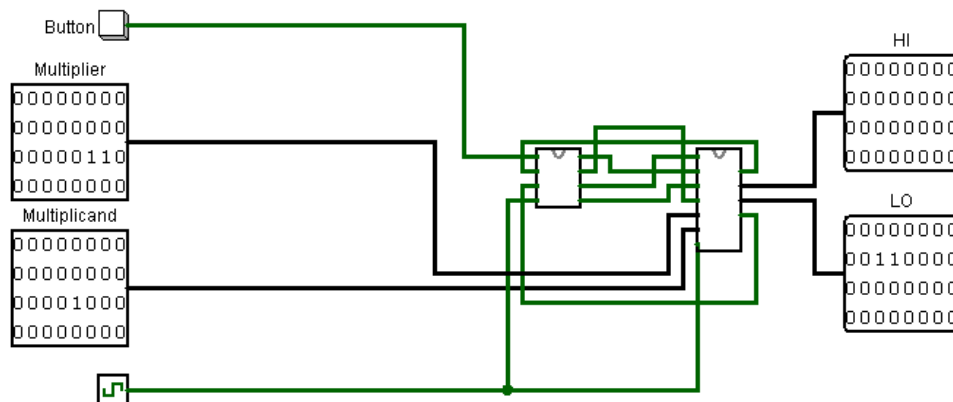


$$2048 * 1536 = 3145728$$

3-

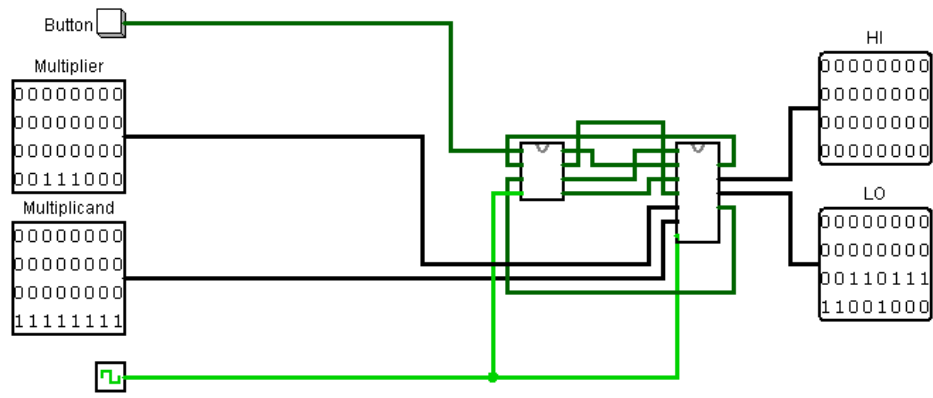

$$255 * 56 = 14280$$


4-

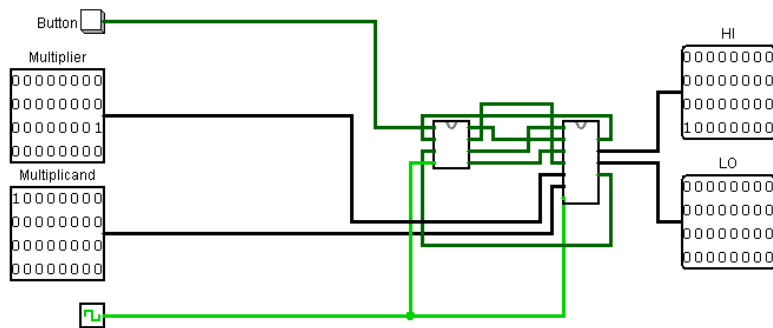

$$2^{31} * 2^8 = 2^{39}$$




5-

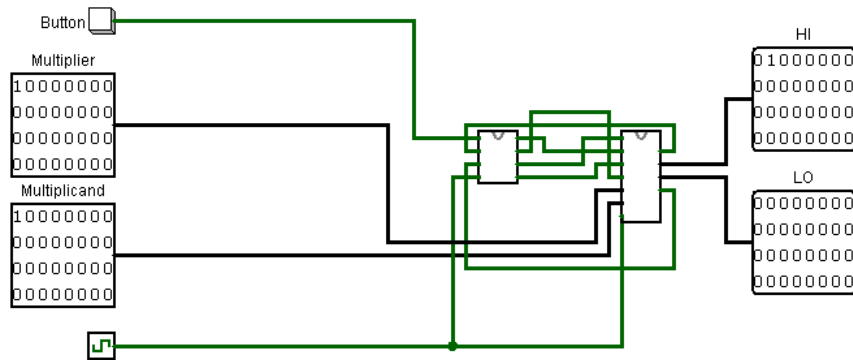

$$2^{31} * 2^{31} = 2^{62}$$

6-

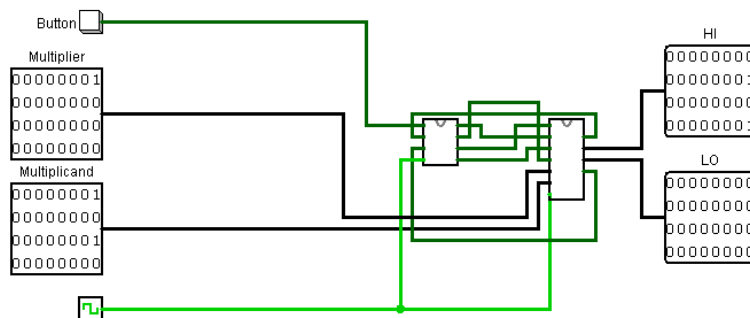

$$2^{24} * (2^{24} + 2^8) = 2^{48} + 2^{32}$$